



**SAKARYA**  
UNIVERSITY

**SAKARYA UNIVERSITY**  
**PHYSICS LABORATORY II**  
**2019-2020**

***EXPERIMENT REPORT***

***EXPERIMENT NUMBER***    2

***EXPERIMENT NAME***        Kirchhoff's Laws and Wheatstone Bridge

***DATE***

***GROUP NUMBER***

***GROUP MEMBERS***

***DEPARTMENT:***

***NAME-SURNAME:***

***NUMBER:***

***DELIVERY DATE:***

***REPORT SCORE:***

## Measurement and Calculations

1. Draw the electrical circuit. Show the features  $\{R(\Omega), V(\text{volt}), i(\text{amper})\}$  of the each circuit elements on the figure. (20 p.)

2. Calculate the rheostat value  $R_4$  which balances the Wheatstone bridge. (25 p.)

3. Write the following quantities together with their units. (15 p.)

d (Whole length of rheostat) = .....

R (All resistance of rheostat) = .....

L (Rheostat length balances the Wheatstone bridge) = .....

4. Obtain the rheostat value  $R_4$ , which balances the Wheatstone bridge, experimentally from the equation of  $R_4 = \frac{LxR}{d}$ . (25 p.)

5. Calculate % error by comparing the theoretical and experimental values of  $R_4$  (15 p.)