



SAKARYA
UNIVERSITY

SAKARYA UNIVERSITY
PHYSICS LABORATORY II
2019-2020

EXPERIMENT REPORT

EXPERIMENT NUMBER 3

EXPERIMENT NAME Finding RC time constant

DATE

GROUP NUMBER

GROUP MEMBERS

DEPARTMENT:

NAME-SURNAME:

NUMBER:

DELIVERY DATE:

REPORT SCORE:

Measurements and Calculations

1. Calculate $-\ln(I)$ for each current value and fill it in the table. Also find the time until each current value is reached and fill it in the table. (20 p.)

I (A)	$-\ln(I)$	t(s)
$10,0 \cdot 10^{-6}$		0
$9,5 \cdot 10^{-6}$		
$9,0 \cdot 10^{-6}$		
$8,5 \cdot 10^{-6}$		
$8,0 \cdot 10^{-6}$		
$7,5 \cdot 10^{-6}$		
$7,0 \cdot 10^{-6}$		
$6,5 \cdot 10^{-6}$		
$6,0 \cdot 10^{-6}$		
$5,5 \cdot 10^{-6}$		
$5,0 \cdot 10^{-6}$		
$4,5 \cdot 10^{-6}$		
$4,0 \cdot 10^{-6}$		
$3,5 \cdot 10^{-6}$		
$3,0 \cdot 10^{-6}$		
$2,5 \cdot 10^{-6}$		
$2,0 \cdot 10^{-6}$		
$1,5 \cdot 10^{-6}$		
$1,0 \cdot 10^{-6}$		
$0,5 \cdot 10^{-6}$		

2. Using the data in the table, plot the $-\ln(I) - t$ chart on millimeter paper. (please, add the chart your report) (30 p.)
3. Find the RC time constant from the slope of the line from graph. (Please, show clearly how you find the slope on the line) (30 p.)

RC (exp.) =

4. Calculate the theoretical value of the RC time constant. ($C = 60 \mu\text{F}$ ve $R = 1 \text{ M}\Omega$) (10 p.)

RC (theo.) =

5. Find the % error using theoretical and experimental RC time constant values. (10 p.)